

1. (a) Assuming ideal opamp, determine the transfer function of KHN biquad high pass filter. Design a KHN circuit to realize a high pass function with  $f_o = 10KHz$  and  $Q = 2$ , assume the integrators have same resistors and capacitors, with  $C = 1nF$ . What is the value of high frequency gain obtained? What is the centre frequency gain of bandpass function that is simultaneously available at the output of the first integrator?

**Solution:**

$$\frac{V_{out}}{V_{in}}(S) = \frac{b_2 S^2}{S^2 + \frac{\omega_n}{Q} S + \omega_n^2} \quad (1M)$$

$$V_{out}(S) = b_2 V_{in}(S) - \frac{\omega_n}{Q} \frac{1}{S} V_{out}(S) - \frac{\omega_n^2}{S^2} V_{out}(S)$$

(b) fl;kajs

(M5:CO3:L3)

2. Assuming ideal opamp, determine the transfer function of KHN biquad high pass filter. Design a KHN circuit to realize a high pass function with  $f_o = 10KHz$  and  $Q = 2$ , assume the integrators have same resistors and capacitors, with  $C = 1nF$ . What is the value of high frequency gain obtained? What is the centre frequency gain of bandpass function that is simultaneously available at the output of the first integrator?

(M10:CO3:L4)

3. (a) In the two-stage op-amp of Fig.a,  $(W/L) = (50/0.5)$  for all transistors except for  $M_5$ , for which  $(W/L)_5 = (72/0.5)$ . Also,  $I_{D7} = 1mA$  and the output branch is biased at  $0.5mA$ . Given  $V_{DD} = 3V$ ,  $K_n = 360\mu A/V^2$ ,  $K_p = 90\mu A/V^2$ ,  $\lambda_n = 0.1V^{-1}$ ,  $\lambda_p = 0.1V^{-1}$ ,  $V_{Tn} = 0.7V$  and  $V_{Tp} = -0.8V$ .
- Determine the CM level at nodes X and Y.
  - Calculate the maximum output voltage swing.
  - Calculate the total gain of the op-amp.

(M7:CO2:L6)

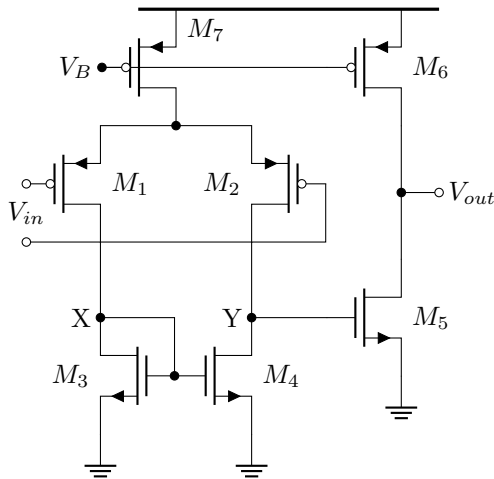


Fig.a

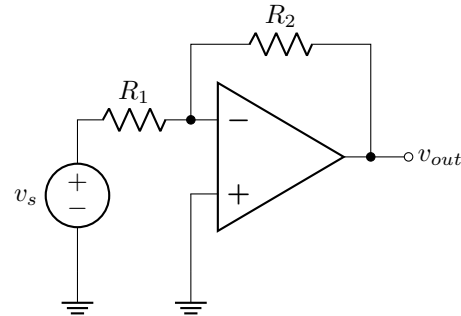


Fig.b

- (b) If the above op-amp is used in a closed loop configuration (as shown in Fig.b) with  $R_1 = 1k\Omega$  to achieve a closed-loop DC gain of  $-3$ , calculate the value of  $R_2$  that is required to achieve the required closed-loop gain and the gain error that results due to finite open-loop gain.

(M3:CO3:L2)